

---

## Lesson 3

# Digital Control of Three-Phase DC/AC Converters: Current Control Techniques

## Linear Current Control

---

## Current Sensing

- **Current sensing is normally not a troublesome part of the control design. Several solutions can be adopted:**
  - **resistive shunts;**
  - **current transformers;**
  - **LEM (Hall effect based) sensors.**
- **In DC/DC converter applications, resistive shunts or current transformers, if isolated sensing is required, are the preferred, cost-driven choices.**

---

## Current Sensing


- In VSI's applications (such as drives, rectifiers, UPS's), the cost of three (or two if the system has only three wires) Hall effect sensors is normally reasonable.
- This solution greatly simplifies the design of the current control system, providing isolated and relatively large bandwidth ( $\gg 100$  kHz) current sensing.
- Only simple filtering (high frequency noise) and level adjusting circuitry (to get A/D converter compatible voltage ranges) are normally required.

---

## Linear Current Control

- The simplest way of achieving current regulation in a DC/AC or AC/DC power converter is to employ linear regulators (usually of PI type).
- The design and digital implementation of such regulators is quite straightforward and normally effective, unless demanding static and dynamic performance specifications are given for the current loop.
- Some basic guidelines can be given for a successful implementation.

## Linear Current Control

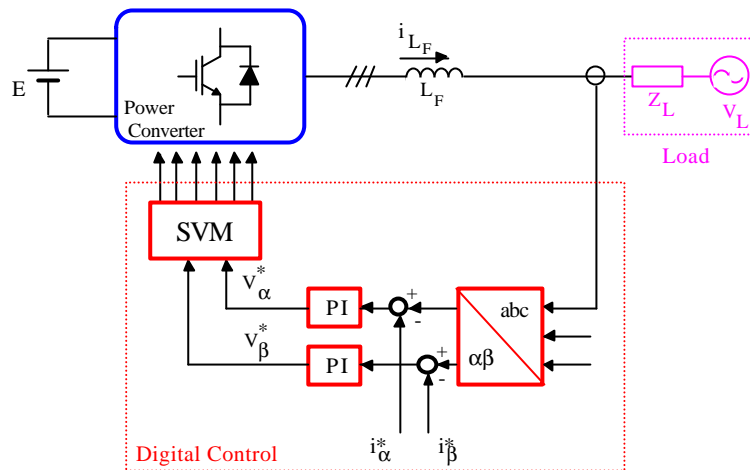

### Typical control set-up

October 1999

Simone Buso - University of Padova - Lesson 3

5

## Control Design


- **The choice of the controller (and its design) in general depends on the particular converter load.**
- **It is very common that the dynamic behaviour of the load, in the typical frequency range of interest for current control design, is almost purely inductive.**
- **Possible capacitive filters (e. g. in UPS applications) normally exhibit a negligible impedance in the vicinity of the switching frequency.**

October 1999


Simone Buso - University of Padova - Lesson 3

6

## Typical Inverter Loads

 


 Can represent both a drive or an active filter application or rectifier (with a suitable choice of the model parameters).



Represents the typical UPS application.

## Design Example

 

$$C = 100 \mu\text{F},$$


$$R = 0.1 \Omega,$$

$$L = 2 \text{ mH}$$

$$V_{dc} = 400 \text{ V}$$

$$f_{sw} = 10 \text{ kHz}$$

## Typical Inverter Loads

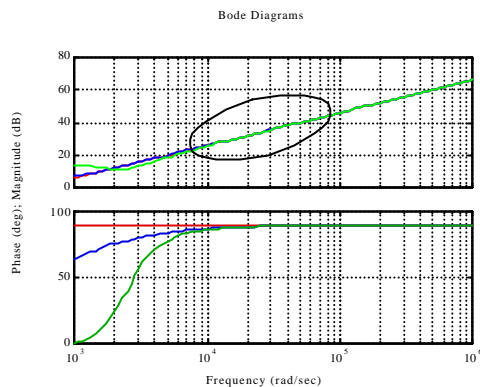

In the area around the possible current loop cross-over frequency the inverter load is 'seen' as almost purely inductive. The controller design can be very simple.

- L - C load (UPS)
- R - L load (drives)
- Purely inductive load

## Control Design

- The typically adopted controller structure is the proportional-integral (PI).
- The design of the controller parameters (proportional and integral gains) is straightforward in the continuous time domain.
- The discretization of the controller can be easily performed as the final step, according to one of the various integration methods (e.g. Euler or trapezoidal integration).
- There is normally no reason to consider more sophisticated approaches.

---

## Control Design

A simple procedure to design a PI regulator can be the following (continuous time domain):

- Set the proportional gain  $k_p$  to:

$$k_p = 2 \cdot \omega_{cr} \cdot L / V_{dc}$$

to get the desired cross-over frequency  $\omega_{cr}$ ;

- Set the integral gain  $k_i$  to:

$$k_i = k_p \cdot \omega_{cr} / \tan(m_f)$$

so as to get the desired phase margin  $m_f$

The gain of the power converter is assumed to be  $V_{dc}/2$  (no PWM delay effect) and the load to be purely inductive. Transducer gains are not taken into account.


---

## Control Design

- It is important to take into account, even at this early stage of the design, that the final controller is going to be digitally implemented.
- In particular, the delay of the sample and hold (@  $T/2$ , where  $T$  is the sampling period) must be considered designing the continuous time controller.
- The required phase margin has to be oversized to cope with such delay. A rule of thumb is to increase  $m_f$  by at least  $20^\circ$  (for a control cross-over frequency about a decade lower than the sampling one).

## Control Design

Bode Diagrams

 


**Open loop gain for the considered example with the suggested design. Almost the same crossover frequency and phase margin is achieved.**

- L - C load (UPS)**
- R - L load (drives)**
- Purely inductive load**

## Control Design

Step Response

 

**Closed loop step response for the considered example with the suggested design. Almost the same performance is achieved in the three cases.**

- L - C load (UPS)**
- R - L load (drives)**
- Purely inductive load**

---

## Control Design

- The continuous time controller must be turned into an equivalent discrete time controller;
- This can be easily done by substituting continuous integrators with discrete ones, according to any discrete time integration method;
- Using Euler's integration method, this is equivalent to set:


$$s = (1-z^{-1})/T \quad T = \text{sampling period,}$$

in the original controller's Laplace transform.

---
 
## Control Design

- In the case of a PI controller, this is equivalent to the following block diagram:



where  $k'_i = k_i \cdot T$  (sampling period).



---

## Control Design

- The block diagram directly leads to the following implementation of the digital PI regulator:

$$y(k) = k_p \cdot u(k)$$

$$i(k) = i(k-1) + k'_i \cdot u(k)$$

$$y(k) = y(k) + i(k)$$

which normally requires only a few clock cycles to be calculated (2 products and 2 sums).

---

## Control Design

- It is important to notice that this procedure is approximated. The discretization process 'warps' the frequency response of the controller, especially for frequencies which are close to the sampling frequency.
- As a rule of thumb, at least a decade must be taken between the sampling frequency and the highest frequency of interest (normally the loop cross-over frequency).
- If the specs require a less conservative design, different synthesis strategies ought to be considered.

---

## Switching Frequency / Sampling Frequency


- The **current waveforms in VSI's exhibit a significant high frequency harmonic content due to the PWM modulation (ripple).**
- The **current control loop is normally needed to control the average value of the converter's currents.**
- **Sampling at very high frequencies to reconstruct the complete current waveform (including the ripple) is therefore not necessary.**

---

## Switching Frequency / Sampling Frequency

- **On the other hand, sampling at high frequencies increases the achievable current loop bandwidth.**
- **Therefore, a simple or double sampling per modulation period is normally adopted.**
- **The basic idea is that sampling and switching must be synchronized to avoid errors.**
- **Currents are typically sampled at the beginning and in the middle of the modulation period.**

## Switching Frequency / Sampling Frequency

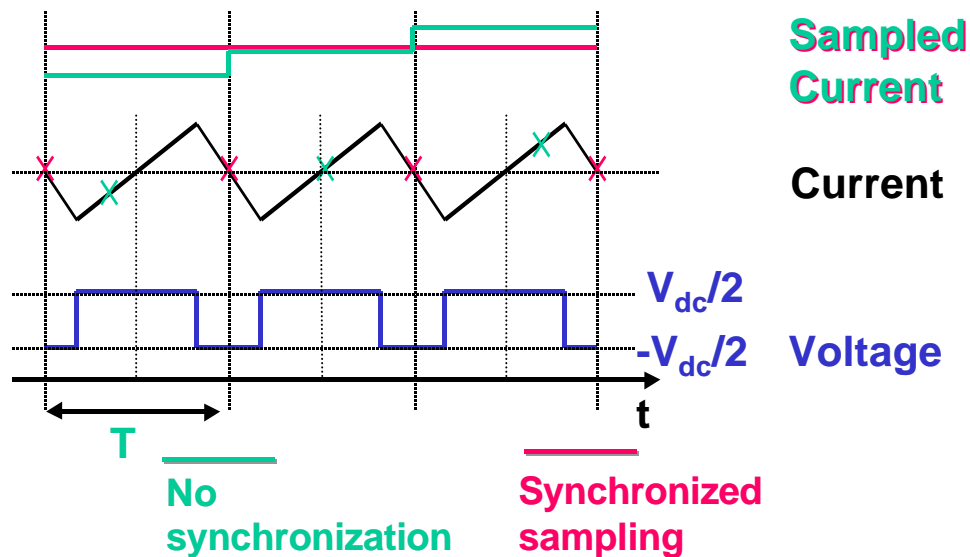

October 1999

Simone Buso - University of Padova - Lesson 3

21

## Control Design

- **Continuous time synthesis and successive discretization is a simple, but approximate, procedure, requiring particular caution in the design of the closed loop bandwidth.**
- **In general, the design is more conservative than direct digital design.**
- **Sampling frequency does not need to be much higher than the switching frequency: practically the former is set equal to or twice the latter.**
- **It is fundamental that sampling and switching are synchronized to avoid aliasing errors.**

October 1999


Simone Buso - University of Padova - Lesson 3

22

---

## Control Design
 
### Time domain simulation with PWM modulation




The controller's response is good but some overshoot is visible at the end of saturated mode of operation. This can be improved by anti wind-up implementation.

---

## Control Design

- The overshoot is due to the integral part of the controller, which gets “overcharged” during the saturated mode of operation. This has no relation with the open loop phase margin.
- As a consequence, a negative error will be needed to remove the accumulated positive error. This generates the overshoot.
- A good solution to this problem is the so-called anti wind-up action.
- This basically consists in the dynamic saturation of the integral part of the controller.

## Control Design

 


**Modified PI controller with anti wind-up action.**  
**The control now is non-linear. Note the position of the saturation function.**

$$|L(k)| = Y_{\max} - |k_p \cdot u(k)|$$

**In any control cycle, the dynamic saturation limit L is calculated, so as to keep the control's output y within the limit  $Y_{\max}$ .**

## Control Design
 
### Time domain simulation with PWM modulation



**The controller's response is now free of overshoot. The control action is purely proportional until saturation is over.**

---

## Three Phase Implementation

- The control of three-phase VSI's requires, in general, three independent, but normally identical, current controllers.
- If the neutral is not connected, currents are not independent, and therefore it is possible to control only two currents out of three.
- It is therefore also possible to:
  - ✓ use Park's transformation to move from the  $a, b, c$  to the  $a, b$  fixed reference frame;
  - ✓ use  $d, q$  rotating reference frame.

---


## Three Phase Implementation

- The use of  $d, q$  rotating reference frame is quite common in adjustable speed drive applications to simplify the dynamics of the electrical machine.
- It can also be used in rectifier, UPS or active filter applications of VSI's. The advantage is the possibility of controlling very precisely the fundamental component of any variable.
- In any case, the  $d, q$  transformation modifies the dynamic equations of the system. This must be considered in the controller's design.

## Implementation Example

- In the following, an **implementation example** will be given with a **fixed point DSP**.
- The employed system is the so-called **VeCon system** manufactured, but not sold on the market, by a consortium of european companies, such as **Siemens and ABB**.
- In the **early 90's**, when this system first became available, it represented the **first DSP system** specifically designed for **power converters' control tasks**.

## Implementation Example

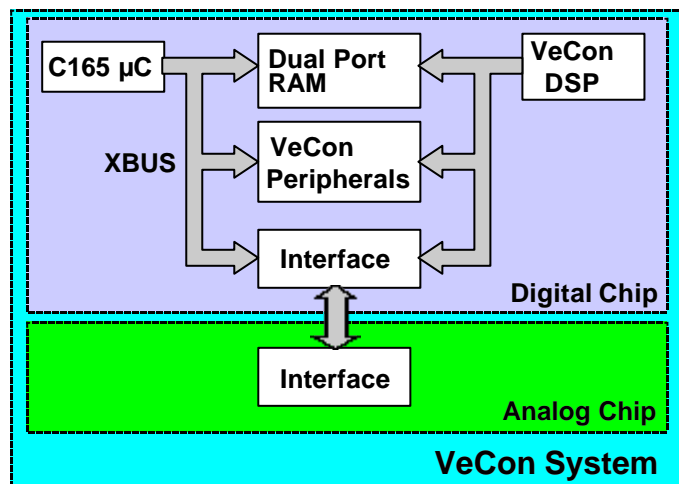

## Structure of the VeCon System

---

## Implementation Example

### C165 microcontroller:

- **16-bit CPU** with extended instruction set (compared to 80C166)
- **16 Mbyte** address space
- **2 kbyte** RAM
- **32 interrupt sources** (8 @ 50ns sampling rate)
- **8 peripheral event controllers**
- **asynchronous\synchrous interfaces**

---

## Implementation Example

### VeCon DSP:

- **20 MHz** clock
- **ALU with three 32-bit registers** for arithmetic operations
- **16\*16 bit multiplier** for signed fractional multiplication (MACL: 100ns)
- **1024 24-bit locations** internal program memory
- **two data memories** each with **128 16-bit locations**



---

## Implementation Example

### Peripheral Units:

- Position sensor evaluation
- Inverter triggering (PWM)
- Interface to Analog Chip
- Synchronous serial interface

---


## Implementation Example

### The analog ASIC includes:

- 3 12-bit 10 $\mu$ s A/D converters each with 4 multiplexed inputs
- 7 comparators to check input signals sign
- 4 hysteresis comparators to check overcurrent condition
- 6-bit D/A converters to set overcurrent limit
- 4 additional sample & hold circuits

---

## Implementation Example

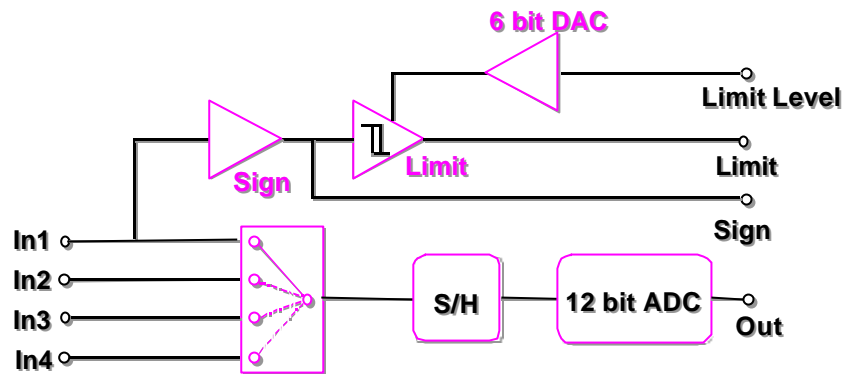

## Analog to Digital Conversion Unit

---

## Implementation Example

- The program calculates the **current references** in the **a, b** reference frame. This reduces the number of accesses to the **sin(x)** look-up table.
- The **current control** is performed on the **a, b, c** reference frame and, consequently, **a, b - a, b, c** transformation is used.
- **Two PI controllers** are used to implement the **current regulation (3 wires)**.
- **Post processing of the duty-cycles with third harmonic injection** is used to implement **SVM**.

---

## Implementation Example

```
; Alfa-Beta Current Reference Generation
;
MOVE      X1,INCREM ; Load increment
MOVE      A1,THETA  ; Load current result in the
; accumulator
ADD  A1,X1          ; Sum THETA + INCREM and
MOVE      THETA,A1  ; move the result in THETA
;
SIN
MOVE      X0,THETA  ; Calculate sin
TAB SINTAB,7      ;
MOVE      IA_REF,A1 ; Store it in IA_REF=Sin(THETA)
MOVE      A1,THETA  ;
MOVE      X1,HALF   ; THETA + 90 degrees
ADD       A1,X1     ;
MOVE      X0,A1     ;
TAB SINTAB,7      ;
MOVE      IB_REF,A1 ; IB_REF=Sin(THETA+90)
```

October 1999

Simone Buso - University of Padova - Lesson 3

37

---

## Implementation Example

```
; Alfa-Beta -> U,V,Z Transform
;
TRSF23
MOVE      X1,TWO_THIRDS ;
MOVE      Y1,IA_REF      ;
MUL X1,Y1 X0,SIN_60    ;
MOVE      IU_REF,A1      ; IU_REF = 2/3*IA_REF
MOVE      Y0,IB_REF      ;
MUL X0,Y0              ;
MOVE      X0,A1          ;
MUL X0,X1 Y0,SIN_30    ;
MOVE      X0,A1          ;
MOVE      Y1,IU_REF      ;
MUL Y0,Y1              ;
ADD -A1,X0             ;
MOVE      IV_REF,A1      ; IV_REF = 1/SQRT(3)*IB_REF
; -1/3*IA_REF
```

October 1999

Simone Buso - University of Padova - Lesson 3

38

## Implementation Example

```

PI_U                                     ; PI phase U
MOVE      X1,IU_ANA ;
MOVE      A1,IU_RF  ;
SUBL      A1,X1     ;
MOVE      ERROR,A1 ; Control input variable
MOVE      Y1,KPU    ; Proportional gain
MOVE      X1,A1     ;
MUL  X1,Y1  X0,UCOMP ; Proportional part OK
ADDL  A1,X0  X0,LIMPOS ; Feed-forward compensation
LIMS  A1,X0  Y0,LIMNEG ;
LIMI  A1,X0  PROPU,A1 ; Anti wind-up for the
MOVE      A,INTEGU ; integral part
MOVE      Y1,KIU   ;
MACL  X1,Y1  ;
LIM  X0,Y0  X1,PROPU ;
ADDL  A1,X1  INTEGU,A ; N.B. The move is executed
                                           ; before the add
MOVE      UREF,A1  ; end PI phase U

```

October 1999

Simone Buso - University of Padova - Lesson 3

39

## Implementation Example

```

MODULA                                     ; SVM part of the program
MOVE      Y0,UREF ;
MOVE      Y1,VREF ;
HAR3
MOVE      Y1,A1   ;
MOVE      THIRD,Y1 ;
;
; Switching instants
;
MOVE      X0,MODE_U ; Load PWM mode
MOVE      Y1,THIRD ; Calculate 'third harmonic'
MOVE      Y0,TMOD_1 ; Limit to TMOD - 1 (PWM)
MOVE      A1,UREF ; Load voltage reference
MOVE      X1,TMOD_2 ;
ADD      A1,Y1   ; Load third harmonic
PWM      A1,X1   ; Calculate instant TU1
LIMU     A1,Y0   ; Limit TU1 to TMOD_1
MOVE      TU1,A1 ; Store the result

```

October 1999

Simone Buso - University of Padova - Lesson 3

40

---

## References

- [1] L. Rossetto, L. Malesani, P. Tenti, S. Buso, A. Pollmann: "Fully Digital Control of a Three Phase UPS by VeCon Integrated Controller" IEEE Industry Applications Society (IAS) Annual Meeting, Orlando, October 8-12, 1995, pp. 2663-2669.
- [2] E. Kiel and W. Schumacher, "VeCon: A High-Performance Single-Chip-Servocontroller for AC Drives", IPEC Conf. Proc., 1995, pp. 1284-1289.